

Electric Machine Control

Chapter 3

d,q Models for Solid State Power Converters

Woei-Luen Chen

3.1 Introduction

- ✱ Combining machine-converter modelling by the dq reference frame
 - VSI dq models in a stationary reference frame
 - Six-step operation
 - PWM operation
 - CSI dq models in a stationary reference frame
 - VSI dq models in a synchronous reference frame
 - Example
 - Stationary/ synchronous RF dq models of a VSI/CSI
 - Simplified stationary/ synchronous RF dq models of a VSI/CSI
 - Including the effects of the dc link filter
 - Neglecting the effect of the inverter harmonics
 - Dc link variables referred to the induction motor stator

3.2 d,q Model for VSI

❁ Six step operation

❑ Consider first the connection 612

$$\begin{cases} v_{ab} = -v_{ca} = v_i & (3.2-4) \end{cases}$$

$$\begin{cases} v_{bc} = 0 & (3.2-5) \end{cases}$$

$$\begin{cases} i_{as} = i_i & (3.2-6) \end{cases}$$

$$\begin{cases} i_{as} + i_{bs} + i_{cs} = 0 & (3.2-7) \end{cases}$$


$$\begin{cases} v_{as} + v_{bs} + v_{cs} = 0 & (3.2-8) \end{cases}$$



$$\begin{cases} v_{as} = \frac{1}{3}(v_{ab} - v_{ca}) = \frac{2}{3}v_i & (3.2-9) \end{cases}$$

$$\begin{cases} v_{bs} = \frac{1}{3}(v_{bc} - v_{ab}) = -\frac{1}{3}v_i & (3.2-10) \end{cases}$$
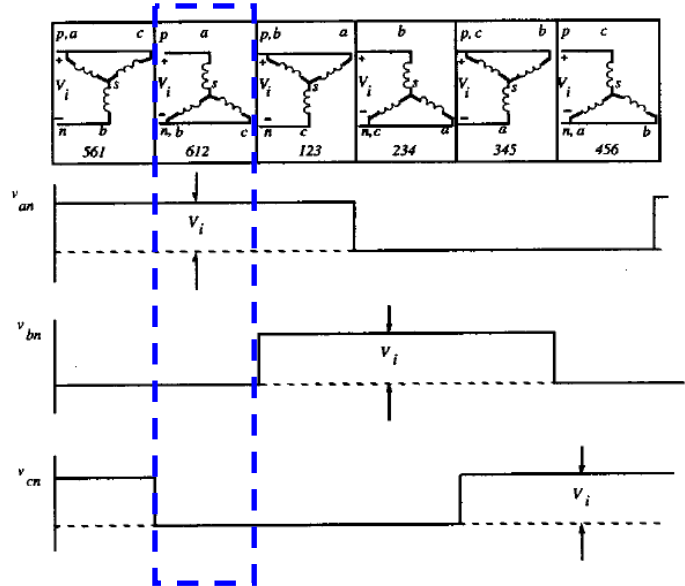
$$\begin{cases} v_{cs} = \frac{1}{3}(v_{ca} - v_{bc}) = -\frac{1}{3}v_i & (3.2-11) \end{cases}$$



3.2 d,q Model for VSI

❁ Six step operation

❑ Consider first the connection 612

$$\begin{cases} v_{as} = \frac{1}{3}(v_{ab} - v_{ca}) = \frac{2}{3}v_i & (3.2-9) \end{cases}$$

$$\begin{cases} v_{bs} = \frac{1}{3}(v_{bc} - v_{ab}) = -\frac{1}{3}v_i & (3.2-10) \end{cases}$$

$$\begin{cases} v_{cs} = \frac{1}{3}(v_{ca} - v_{bc}) = -\frac{1}{3}v_i & (3.2-11) \end{cases}$$

$$\begin{cases} i_{as} = i_i & (3.2-6) \end{cases}$$

$$\begin{cases} i_{as} + i_{bs} + i_{cs} = 0 & (3.2-7) \end{cases}$$



$$\begin{cases} v_{qs}^s = \frac{2}{3}v_i & (3.2-12) \end{cases}$$

$$\begin{cases} v_{ds}^s = 0 & (3.2-13) \end{cases}$$

$$\begin{cases} v_{0s}^s = 0 & (3.2-14) \end{cases}$$





$$\begin{cases} i_{qs}^s = i_i & (3.2-15) \end{cases}$$

$$\begin{cases} i_{ds}^s = \frac{1}{\sqrt{3}}(i_{cs} - i_{bs}) & (3.2-16) \end{cases}$$

$$\begin{cases} i_{0s}^s = 0 & (3.2-17) \end{cases}$$
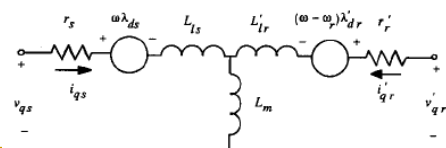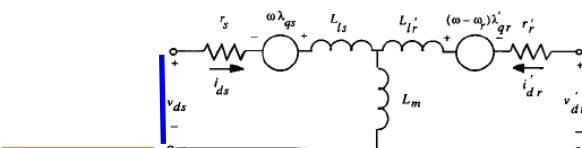
$$\begin{aligned} f_{qs}^s &= \frac{2}{3}f_{as} - \frac{1}{3}f_{bs} - \frac{1}{3}f_{cs} & (3.2-1) \\ f_{ds}^s &= \frac{1}{\sqrt{3}}f_{cs} - \frac{1}{\sqrt{3}}f_{bs} & (3.2-2) \\ f_{0s}^s &= \frac{1}{3}(f_{as} + f_{bs} + f_{cs}) & (3.2-3) \end{aligned}$$



表示什么意思？

Six step operation

1	$-\frac{\pi}{6} < \omega_e t < \frac{\pi}{6}$		$v_{qs}^s = \frac{2}{3}v_i$ $v_{ds}^s = 0$ $i_i = i_{qs}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j0}$
2	$\frac{\pi}{6} < \omega_e t < \frac{\pi}{2}$		$v_{qs}^s = \frac{v_i}{3}$ $v_{ds}^s = -\frac{\sqrt{3}}{3}v_i$ $i_i = \frac{1}{2}i_{qs}^s - \frac{\sqrt{3}}{2}i_{ds}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j\frac{\pi}{3}}$
3	$\frac{\pi}{2} < \omega_e t < \frac{5\pi}{6}$		$v_{qs}^s = -\frac{v_i}{3}$ $v_{ds}^s = -\frac{\sqrt{3}}{3}v_i$ $i_i = -\frac{1}{2}i_{qs}^s - \frac{\sqrt{3}}{2}i_{ds}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j\frac{2\pi}{3}}$
4	$\frac{5\pi}{6} < \omega_e t < \frac{7\pi}{6}$		$v_{qs}^s = -\frac{2}{3}v_i$ $v_{ds}^s = 0$ $i_i = -i_{qs}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j\pi}$
5	$\frac{7\pi}{6} < \omega_e t < \frac{3\pi}{2}$		$v_{qs}^s = \frac{v_i}{3}$ $v_{ds}^s = \frac{\sqrt{3}}{3}v_i$ $i_i = -\frac{1}{2}i_{qs}^s + \frac{\sqrt{3}}{2}i_{ds}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j\frac{4\pi}{3}}$
6	$\frac{3\pi}{2} < \omega_e t < \frac{11\pi}{6}$		$v_{qs}^s = \frac{2}{3}v_i$ $v_{ds}^s = \frac{\sqrt{3}}{3}v_i$ $i_i = \frac{1}{2}i_{qs}^s + \frac{\sqrt{3}}{2}i_{ds}^s$	$v_{qds}^s = \frac{2}{3}v_i e^{j\frac{5\pi}{3}}$

Figure 3.1 d,q equations for the six modes of a VSI

$$v_{qs}^s = \frac{2}{\pi}v_i g_{qs}^s \quad (3.2-18)$$

$$v_{ds}^s = \frac{2}{\pi}v_i g_{ds}^s \quad (3.2-19)$$

$$\frac{\pi}{3}i_i = i_{qs}^s g_{qs}^s + i_{ds}^s g_{ds}^s \quad (3.2-20)$$

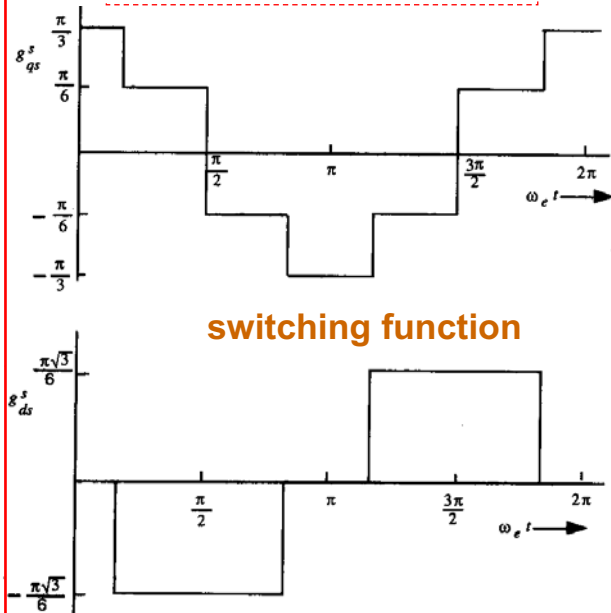


Figure 3.2 The VSI switching functions g_{qs}^s and g_{ds}^s

5

Switching function

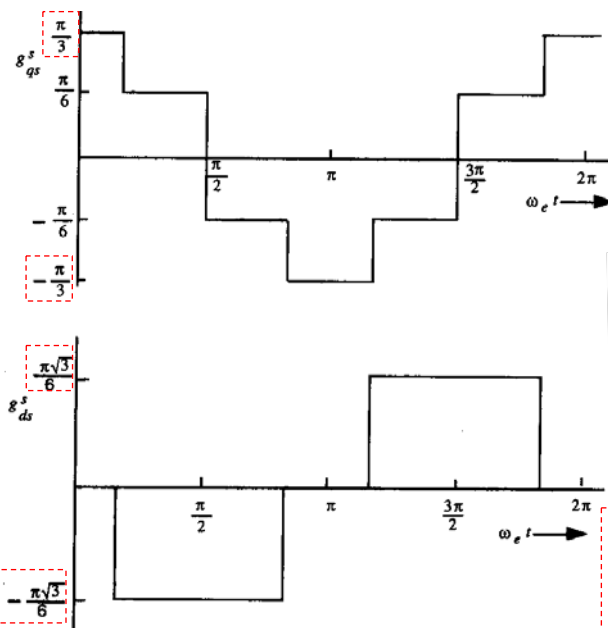


Figure 3.2 The VSI switching functions g_{qs}^s and g_{ds}^s

$$v_{qs}^s = \frac{2}{\pi}v_i g_{qs}^s \quad (3.2-18)$$

$$v_{ds}^s = \frac{2}{\pi}v_i g_{ds}^s \quad (3.2-19)$$

$$\frac{\pi}{3}i_i = i_{qs}^s g_{qs}^s + i_{ds}^s g_{ds}^s \quad (3.2-20)$$

Fourier series of sw fun.

$$g_{qs}^s = \cos\theta_e + \frac{1}{5}\cos 5\theta_e - \frac{1}{7}\cos 7\theta_e - \dots \quad (3.2-21)$$

$$g_{ds}^s = -\sin\theta_e + \frac{1}{5}\sin 5\theta_e + \frac{1}{7}\sin 7\theta_e - \dots \quad (3.2-22)$$



$$v_{qds}^s = v_{qs}^s - jv_{ds}^s = \frac{2}{\pi}v_i (g_{qs}^s - jg_{ds}^s) = \frac{2}{\pi}v_i g_{qds}^s \quad (3.2-23)$$

$$\frac{\pi}{3}i_i = \text{Re} [i_{qds}^s (g_{qds}^s)^\dagger] \quad (3.2-25)$$

Six step operation

$$\underline{v}_{qds}^s = v_{qs}^s - jv_{ds}^s = \frac{2}{\pi}v_i(g_{qs}^s - jg_{ds}^s) = \frac{2}{\pi}v_i \underline{g}_{qds}^s \quad (3.2-23)$$

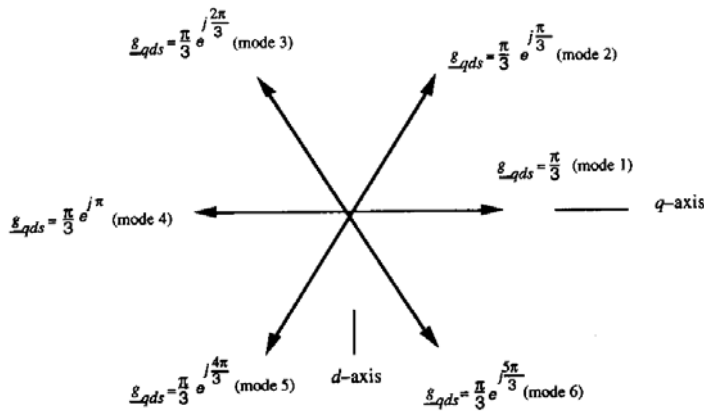


Figure 3.3 The six voltage vectors characterizing VSI operation

(mode 1)

$$\underline{v}_{qds}^s = \frac{2}{3}v_i e^{j0} \quad (3.2-26)$$

(mode 2)

$$\underline{v}_{qds}^s = \frac{2}{3}v_i \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \frac{2}{3}v_i e^{j\pi/3} \quad (3.2-27)$$

Mode 1...6

$$\underline{v}_{qds}^s = \frac{2}{3}v_i e^{j(k-1)\pi/3} \quad k = 1, 2, \dots, 6 \quad (3.2-28)$$

3.3 d,q Model for PWM Operation

Additional states: zero states


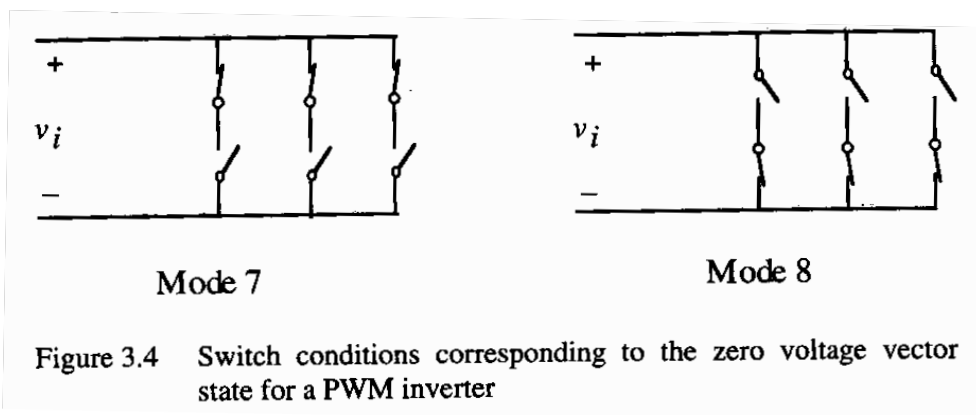


Figure 3.4 Switch conditions corresponding to the zero voltage vector state for a PWM inverter

3.4 d,q Model for CSI

❁ Six step operation

❑ Consider first the connection 12

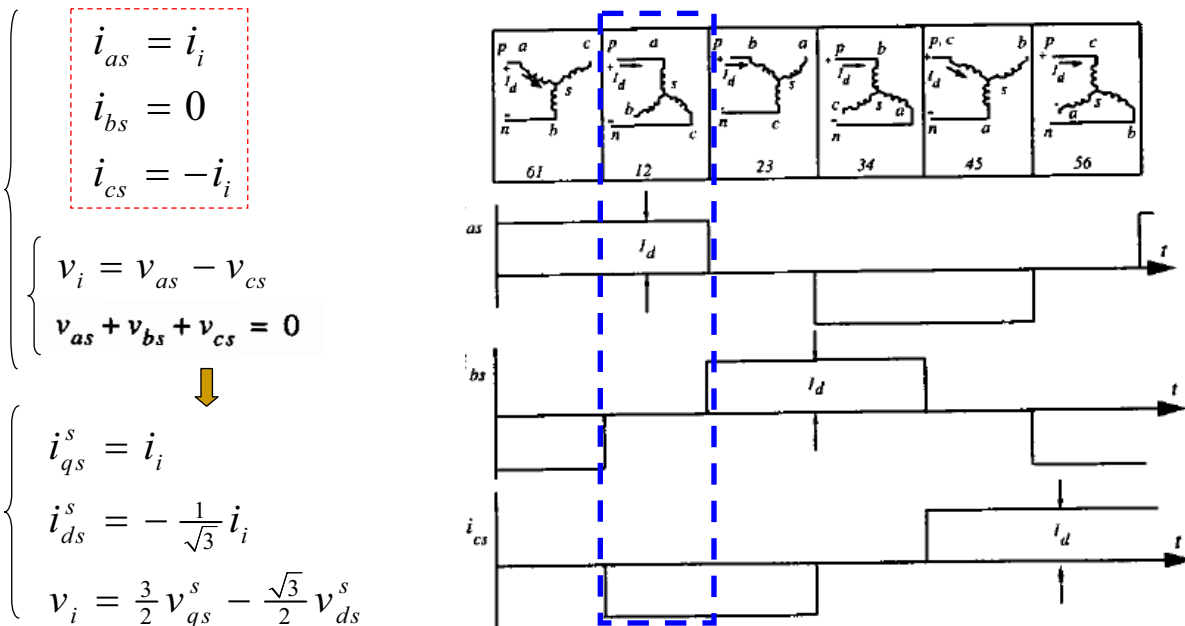

Six step operation

Mode	Time Interval	Connection	dq Equations	Complex Vector Current
1	$0 < \omega_e t < \frac{\pi}{3}$		$i_{qs}^s = i_i$ $i_{ds}^s = -\frac{1}{\sqrt{3}} i_i$ $v_i = \frac{3}{2} v_{qs}^s - \frac{\sqrt{3}}{2} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{\pi}{6}}$
2	$\frac{\pi}{3} < \omega_e t < \frac{2\pi}{3}$		$i_{qs}^s = 0$ $i_{ds}^s = -\frac{2}{\sqrt{3}} i_i$ $v_i = -\sqrt{3} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{\pi}{2}}$
3	$\frac{2\pi}{3} < \omega_e t < \pi$		$i_{qs}^s = -i_i$ $i_{ds}^s = -\frac{1}{\sqrt{3}} i_i$ $v_i = -\frac{3}{2} v_{qs}^s - \frac{\sqrt{3}}{2} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{5\pi}{6}}$
4	$\pi < \omega_e t < \frac{4\pi}{3}$		$i_{qs}^s = -i_i$ $i_{ds}^s = \frac{1}{\sqrt{3}} i_i$ $v_i = -\frac{3}{2} v_{qs}^s + \frac{\sqrt{3}}{2} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{7\pi}{6}}$
5	$\frac{4\pi}{3} < \omega_e t < \frac{5\pi}{3}$		$i_{qs}^s = 0$ $i_{ds}^s = \frac{2}{\sqrt{3}} i_i$ $v_i = \sqrt{3} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{3\pi}{2}}$
6	$\frac{5\pi}{3} < \omega_e t < 2\pi$		$i_{qs}^s = i_i$ $i_{ds}^s = \frac{1}{\sqrt{3}} i_i$ $v_i = \frac{3}{2} v_{qs}^s + \frac{\sqrt{3}}{2} v_{ds}^s$	$i_{qds} = \frac{2}{\sqrt{3}} i_i e^{j\frac{11\pi}{6}}$

$$i_{qs}^s = \frac{2\sqrt{3}}{\pi} h_{qs}^s i_i \quad (3.4-1)$$

$$i_{ds}^s = \frac{2\sqrt{3}}{\pi} h_{ds}^s i_i \quad (3.4-2)$$

$$v_i = \frac{3\sqrt{3}}{\pi} (v_{qs}^s h_{qs}^s + v_{ds}^s h_{ds}^s) \quad (3.4-3)$$

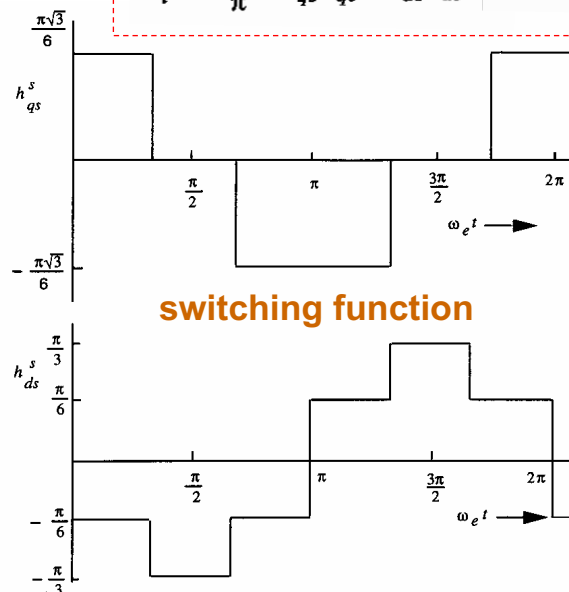


Figure 3.6 The CSI switching functions h_{qs}^s and h_{ds}^s

Switching Function

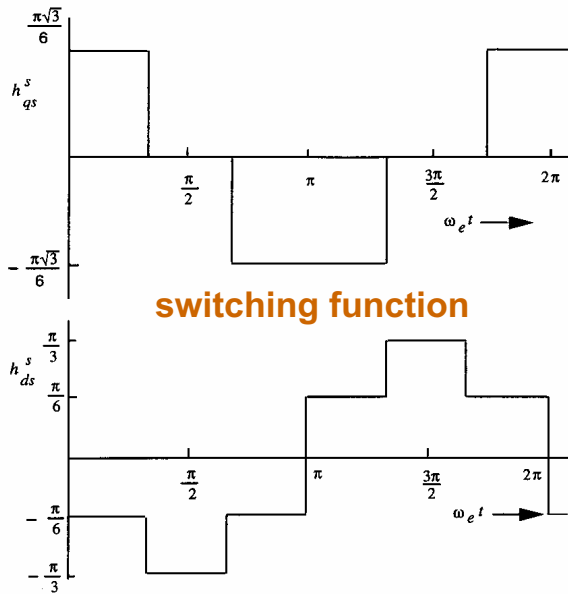


Figure 3.6 The CSI switching functions h_{qs}^s and h_{ds}^s

$$i_{qs}^s = \frac{2\sqrt{3}}{\pi} h_{qs}^s i_i \quad (3.4-1)$$

$$i_{ds}^s = \frac{2\sqrt{3}}{\pi} h_{ds}^s i_i \quad (3.4-2)$$

$$v_i = \frac{3\sqrt{3}}{\pi} (v_{qs}^s h_{qs}^s + v_{ds}^s h_{ds}^s) \quad (3.4-3)$$

Fourier series of sw fun.

$$h_{qs}^s = \cos \omega_e t - \frac{1}{5} \cos 5\omega_e t + \frac{1}{7} \cos 7\omega_e t - \dots \quad (3.4-4)$$

$$h_{ds}^s = \sin \omega_e t - \frac{1}{5} \sin 5\omega_e t + \frac{1}{7} \sin 7\omega_e t - \dots \quad (3.4-5)$$



$$i_{qds}^s = \frac{2\sqrt{3}}{\pi} i_i (h_{qs}^s - j h_{ds}^s) = \frac{2\sqrt{3}}{\pi} i_i h_{qds}^s \quad (3.4-6)$$

$$v_i = \frac{3\sqrt{3}}{\pi} \text{Re} [v_{qds}^s h_{qds}^{s*}] \quad (3.4-7)$$

Six step operation

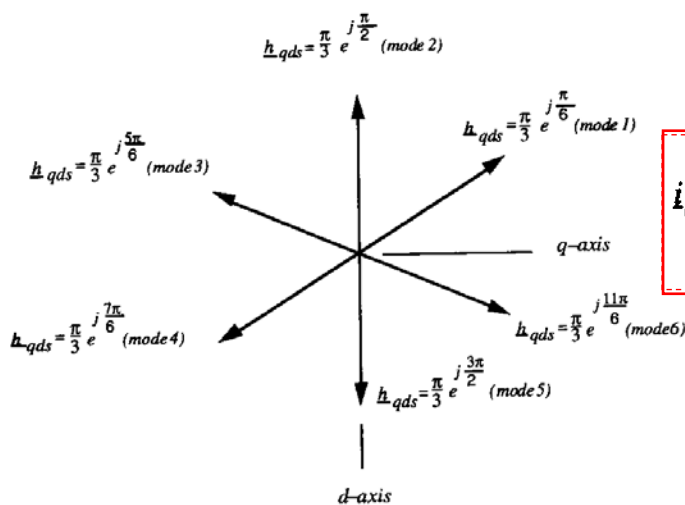


Figure 3.7 The six current vectors characterizing CSI operation

Mode 1...6

$$i_{qds}^s = \frac{2}{\sqrt{3}} i_i e^{j[\pi/6 + (k-1)(\pi/3)]} \quad k = 1, 2, \dots, 6 \quad (3.4-9)$$

3.5 Inverter d,q Models in a Syn.R.F.

- Transform stationary RF to synchronous RF (for VSI)

$$\left\{ \begin{array}{l} v_{qds}^e = v_{qds}^s e^{-j\theta_e} \\ = \frac{2}{\pi} v_i g_{qds}^s e^{-j\theta_e} \\ = \frac{2}{\pi} v_i g_{qds}^e \quad (3.5-5) \end{array} \right. \Rightarrow \left\{ \begin{array}{l} v_{qs}^e = \frac{2}{\pi} v_i g_{qs}^e \quad (3.5-8) \\ v_{ds}^e = \frac{2}{\pi} v_i g_{ds}^e \quad (3.5-9) \\ \frac{\pi}{3} i_i = i_{qs}^e g_{qs}^e + i_{ds}^e g_{ds}^e \quad (3.5-10) \end{array} \right.$$

$$\frac{\pi}{3} i_i = \text{Re} [i_{qds}^e g_{qds}^{e*}] \quad (3.5-6)$$

$$g_{qds}^s = e^{j\omega_e t} + \frac{1}{5} e^{-j5\omega_e t} - \frac{1}{7} e^{j7\omega_e t} - \dots \quad (3.2-24)$$

$$\Rightarrow g_{qds}^e = e^{j(\omega_e t - \theta_e)} + \frac{1}{5} e^{-j(5\omega_e t + \theta_e)} - \frac{1}{7} e^{j(7\omega_e t - \theta_e)} - \dots \quad (3.5-11)$$

- Transform stationary RF to synchronous RF (for CSI)

$$\left\{ \begin{array}{l} i_{qds}^e = i_{qds}^s e^{-j\theta_e} \\ = \frac{2\sqrt{3}}{\pi} i_i h_{qds}^s e^{-j\theta_e} \quad (3.5-14) \\ = \frac{2\sqrt{3}}{\pi} i_i h_{qds}^e \\ v_i = \frac{3\sqrt{3}}{\pi} \text{Re} [v_{qds}^e h_{qds}^{e*}] \quad (3.5-15) \end{array} \right.$$

$$h_{qds}^s = e^{j\omega_e t} - \frac{1}{5} e^{-j5\omega_e t} + \frac{1}{7} e^{j7\omega_e t} - \dots \quad (3.4-8)$$

$$\Rightarrow h_{qds}^e = e^{j(\omega_e t - \theta_e)} - \frac{1}{5} e^{-j(5\omega_e t + \theta_e)} + \frac{1}{7} e^{j(7\omega_e t - \theta_e)} \quad (3.5-16)$$

Switching functions of the VSI and CSI

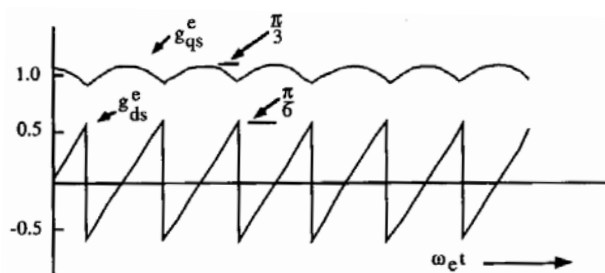


Figure 3.8 The synchronous frame VSI switching functions

$$g_{qs}^e = 1 + \frac{2}{35} \cos 6\omega_e t - \frac{2}{143} \cos 12\omega_e t + \dots \quad (3.5-12)$$

$$g_{ds}^e = \frac{12}{35} \sin 6\omega_e t - \frac{24}{143} \sin 12\omega_e t + \dots \quad (3.5-13)$$

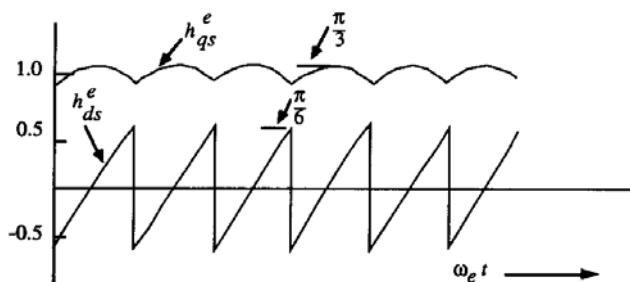


Figure 3.9 The synchronous frame CSI switching functions

$$h_{qs}^e = 1 - \frac{2}{35} \cos 6\omega_e t - \frac{2}{143} \cos 12\omega_e t + \dots \quad (3.5-17)$$

$$h_{ds}^e = -\frac{12}{35} \sin 6\omega_e t - \frac{24}{143} \sin 12\omega_e t + \dots \quad (3.5-18)$$

3.6 Example of Inverter-Induction Motor Models

Stationary RF dq model of a VSI driven IM

怎么理解?

$$v_{qs}^s = \frac{2}{\pi} v_i g_{qs}^s \quad (3.2-18)$$

$$v_{ds}^s = \frac{2}{\pi} v_i g_{ds}^s \quad (3.2-19)$$

$$\frac{\pi}{3} i_i = i_{qs}^s g_{qs}^s + i_{ds}^s g_{ds}^s \quad (3.2-20)$$

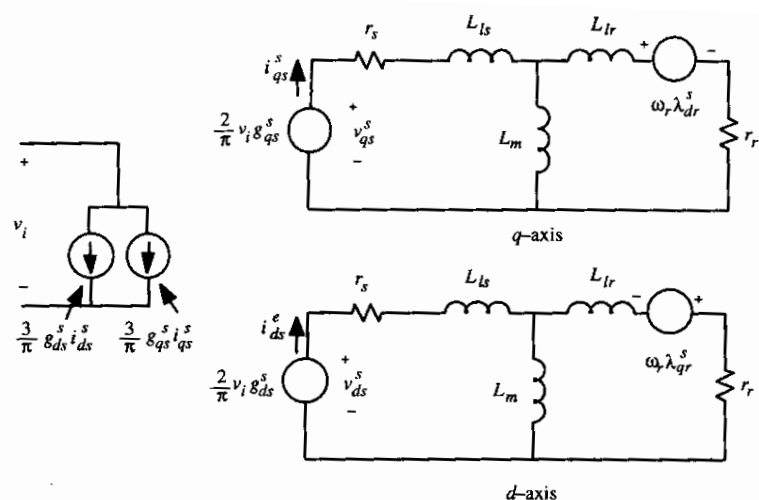


Figure 3.10 Stationary frame d,q model of a VSI driven induction machine

Synchronous RF dq model of a **VSI** driven IM

$$v_{qs}^e = \frac{2}{\pi} v_i g_{qs}^e \quad (3.5-8)$$

$$v_{ds}^e = \frac{2}{\pi} v_i g_{ds}^e \quad (3.5-9)$$

$$\frac{\pi}{3} i_i = i_{qs}^e g_{qs}^e + i_{ds}^e g_{ds}^e \quad (3.5-10)$$

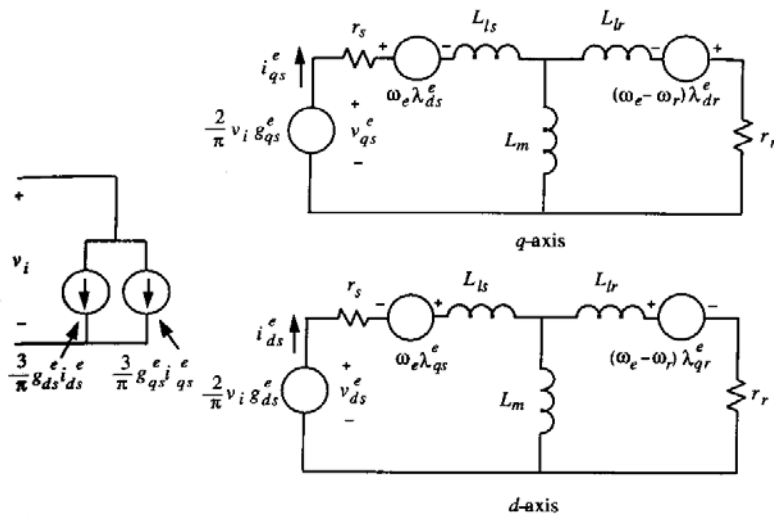


Figure 3.11 Synchronous frame d,q model of a VSI driven induction machine

Stationary RF dq model of a **CSI** driven IM

$$i_{qs}^s = \frac{2\sqrt{3}}{\pi} h_{qs}^s i_i \quad (3.4-1)$$

$$i_{ds}^s = \frac{2\sqrt{3}}{\pi} h_{ds}^s i_i \quad (3.4-2)$$

$$v_i = \frac{3\sqrt{3}}{\pi} (v_{qs}^s h_{qs}^s + v_{ds}^s h_{ds}^s) \quad (3.4-3)$$

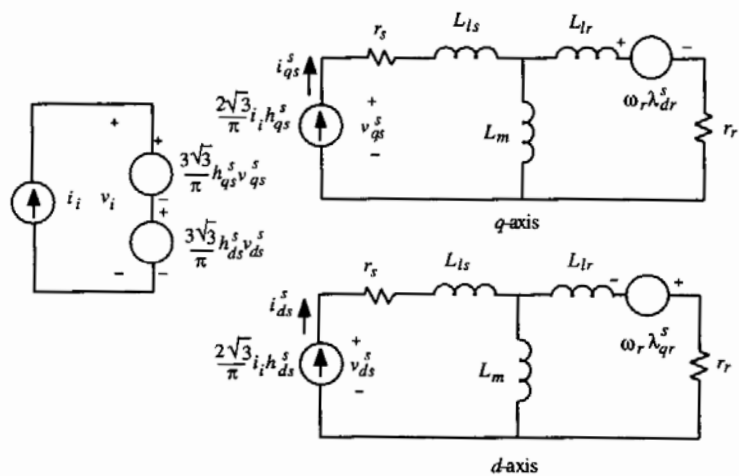


Figure 3.12 Stationary frame d,q model of a CSI driven induction machine

Synchronous RF dq model of a **CSI** driven IM

$$\begin{aligned}
 i_{qds}^e &= i_{qds}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qds}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qds}^e \quad (3.5-14)
 \end{aligned}$$

$$v_i = \frac{3\sqrt{3}}{\pi} \text{Re}[v_{qds}^e h_{qds}^{e*}] \quad (3.5-15)$$

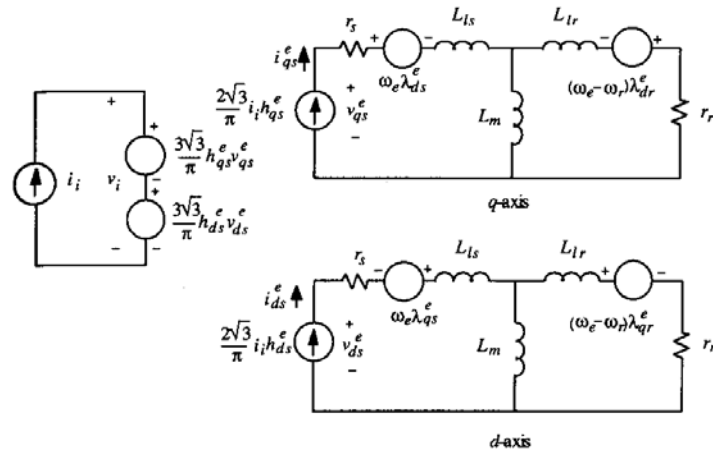


Figure 3.13 Synchronous frame d,q model of a CSI driven induction machine

Simplified Synchronous RF dq model of a **VSI** driven IM (neglect harmonics)

$$v_{qs}^e = \frac{2}{\pi} v_i g_{qs}^e \quad (3.5-8)$$

$$v_{ds}^e = \frac{2}{\pi} v_i g_{ds}^e \quad (3.5-9)$$

$$\frac{\pi}{3} i_i = i_{qs}^e g_{qs}^e + i_{ds}^e g_{ds}^e \quad (3.5-10)$$

w/o harmonics:

$$g_{qs}^e \cong 1$$

$$g_{ds}^e \cong 0$$

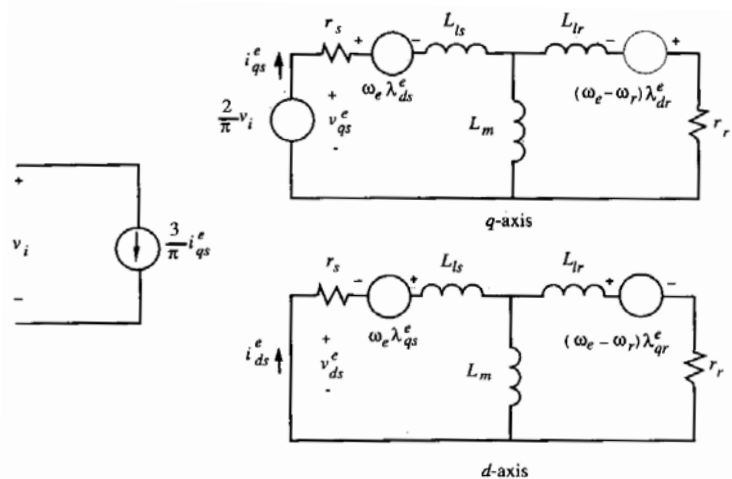


Figure 3.14 Simplified synchronous frame d,q model of VSI driven induction machine

Simplified Synchronous RF dq model of a **CSI** driven IM **(neglect harmonics)**

$$\begin{aligned}
 i_{qds}^e &= i_{qds}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qds}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qds}^e \quad (3.5-14)
 \end{aligned}$$

$$v_i = \frac{3\sqrt{3}}{\pi} \text{Re}[v_{qds}^e h_{qds}^{e*}] \quad (3.5-15)$$

w/o harmonics:

$$h_{qs}^e \cong 1$$

$$h_{ds}^e \cong 0$$

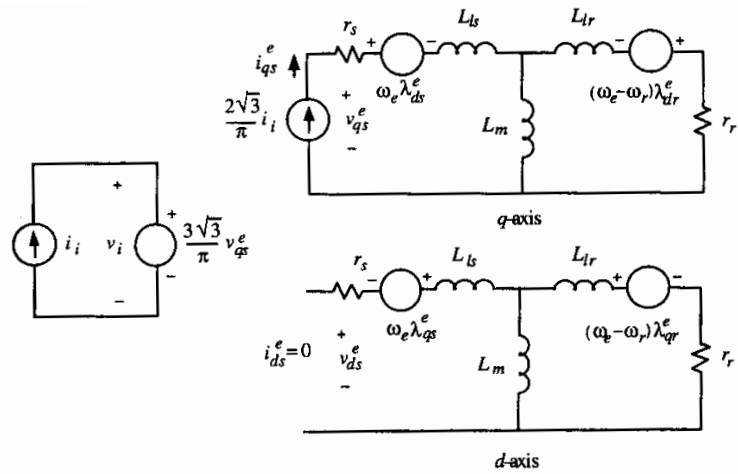


Figure 3.15 Simplified synchronous frame d,q model of CSI driven induction machine

Synchronous RF dq model of a **VSI** driven IM **(Consider the effects of the dc link filter)**

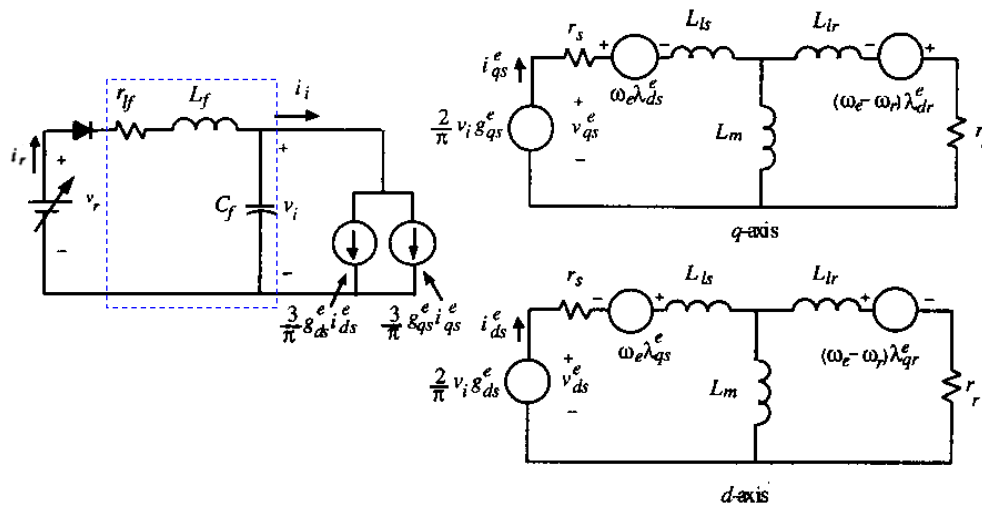



Figure 3.19 Synchronous frame d,q model of VSI driven induction machine including the effects of the dc link filter

◆ Synchronous RF dq model of a **VSI** driven IM (Consider the effects of the dc link filter)

$$v_r = v_i + (r_{lf} + pL_f) i_r \quad i_r > 0 \quad (3.6-6)$$

$$v_r = v_i \quad i_r = 0 \quad (3.6-7)$$
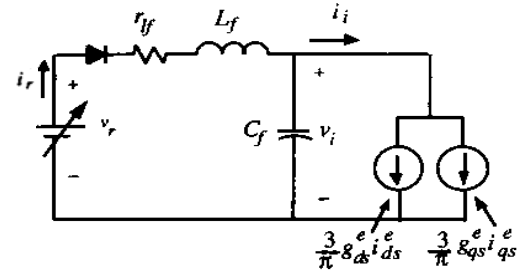
$$v_i = \frac{1}{pC_f} (i_r - i_i) \quad (3.6-8)$$



$$\frac{2}{\pi} v_r = \frac{2}{\pi} v_i + \frac{6}{\pi^2} (r_{lf} + pL_f) \left(\frac{\pi}{3} i_r \right) \quad i_r > 0 \quad (3.6-9)$$

$$\frac{2}{\pi} v_r = \frac{2}{\pi} v_i \quad i_r = 0 \quad (3.6-10)$$

$$\frac{2}{\pi} v_i = \frac{1}{p} \left(\frac{6}{\pi^2 C_f} \right) \left(\frac{\pi}{3} i_r - \frac{\pi}{3} i_i \right) \quad (3.6-11)$$

◆ **Simplified** Synchronous RF dq model of a **VSI** driven IM (Considering the effects of the dc link filter but neglecting the effect of the inverter harmonics)

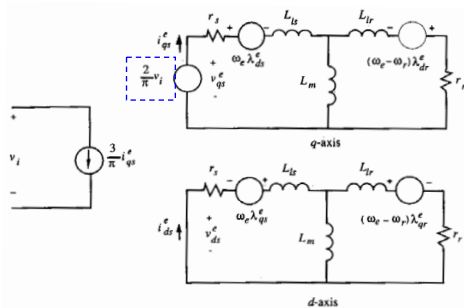


Figure 3.14 Simplified synchronous frame d,q model of VSI driven induction machine

$$v_{qs}^e = \frac{2}{\pi} v_i g_{qs}^e \quad (3.5-8)$$

$$v_{ds}^e = \frac{2}{\pi} v_i g_{ds}^e \quad (3.5-9)$$

$$\frac{\pi}{3} i_i = i_{qs}^e g_{qs}^e + i_{ds}^e g_{ds}^e \quad (3.5-10)$$

w/o harmonics:

$$\begin{aligned} g_{qs}^e &\cong 1 \\ g_{ds}^e &\cong 0 \end{aligned}$$

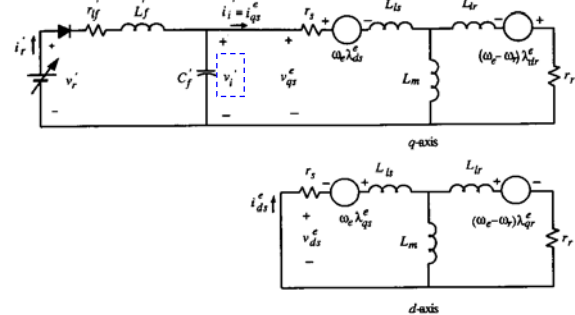


Figure 3.20 Simplified synchronous frame d,q model incorporating the effects of the dc link but neglecting the effect of the inverter harmonics

$$\frac{2}{\pi} v_r = \frac{2}{\pi} v_i + \frac{6}{\pi^2} (r_{lf} + pL_f) \left(\frac{\pi}{3} i_r \right) \quad i_r > 0 \quad (3.6-9)$$

$$\frac{2}{\pi} v_r = \frac{2}{\pi} v_i \quad i_r = 0 \quad (3.6-10)$$

$$\frac{2}{\pi} v_i = \frac{1}{p} \left(\frac{6}{\pi^2 C_f} \right) \left(\frac{\pi}{3} i_r - \frac{\pi}{3} i_i \right) \quad (3.6-11)$$

Simplified Synchronous RF dq model of a **CSI** driven IM (Considering the effects of the dc link filter)

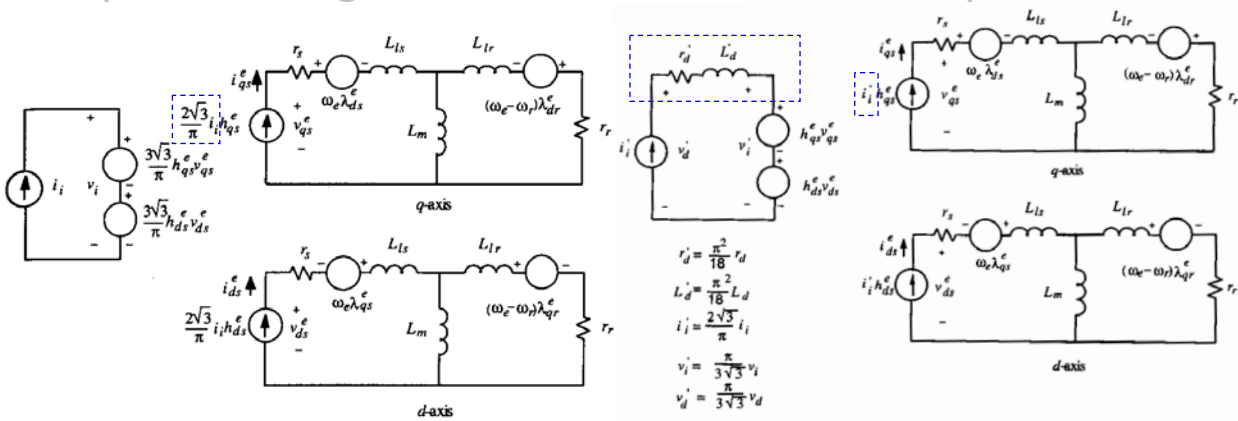


Figure 3.13 Synchronous frame d,q model of a CSI driven induction machine

Figure 3.22 Synchronous frame d,q equivalent circuit of CSI fed induction motor incorporating the effect of the dc link inductor. Link variables referred to the induction motor stator

$$\begin{aligned}
 i_{qds}^e &= i_{qds}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qs}^s e^{-j\theta_e} \\
 &= \frac{2\sqrt{3}}{\pi} i_i h_{qs}^e \quad (3.5-14) \\
 v_i &= \frac{3\sqrt{3}}{\pi} \text{Re} [v_{qds}^e h_{qs}^{e*}] \\
 &\quad (3.5-15)
 \end{aligned}$$

Simplified Synchronous RF dq model of a **CSI** driven IM (Considering the effects of the dc link filter but neglecting the effect of the inverter harmonics)

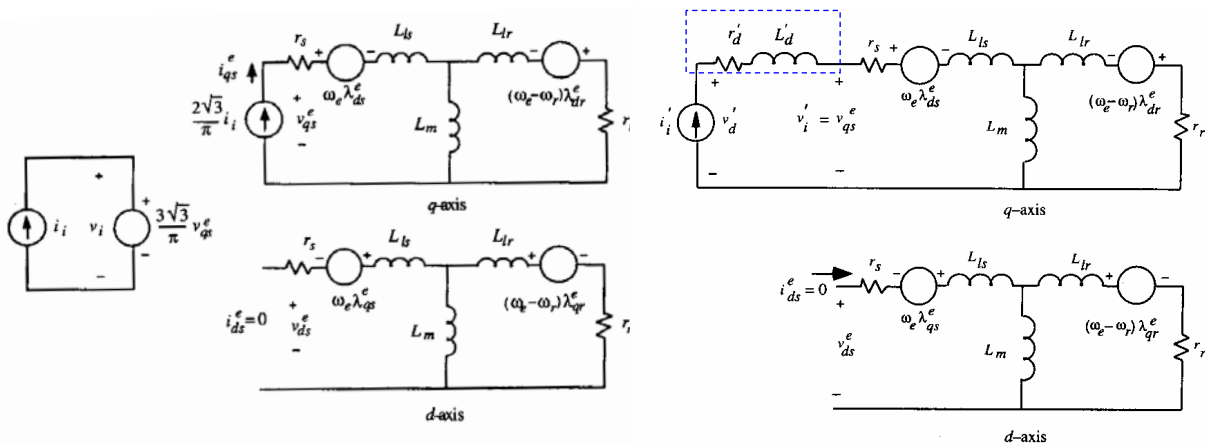


Figure 3.15 Simplified synchronous frame d,q model of CSI drive induction machine

Figure 3.23 Simplified synchronous frame d,q model of CSI fed induction motor incorporating the effects of the dc link but neglecting the effect of the inverter harmonics

Stationary RF dq model of a VSI driven IM

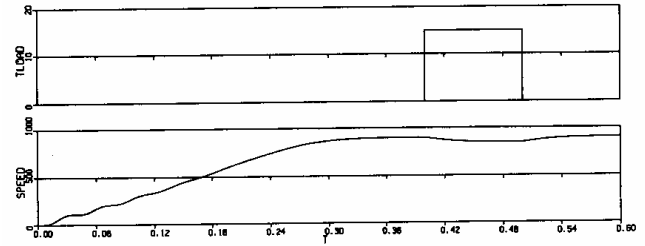
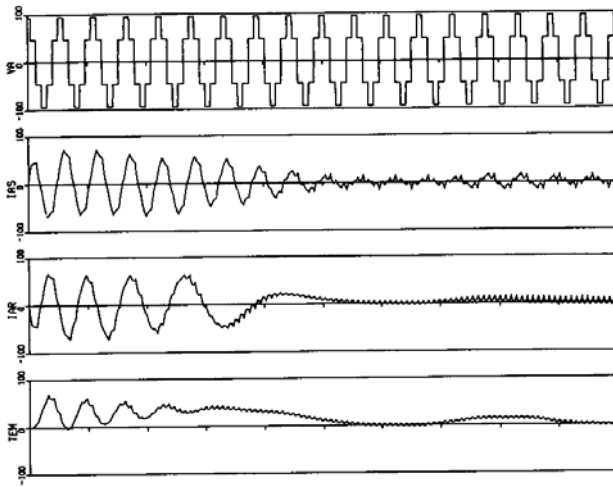


Figure 3.16 Simulation of an induction machine accelerating from rest using a VSI supply with the system represented in the stationary reference frame. The inverter frequency is fixed at 30 Hz. $VA = v_{as} = v_{qs}^s$ (V), $IAS = i_{as} = i_{qs}^s$ (A), $IAR = i_{ar} = i_{qr}^s$ (A), $TEM = T_e$ (N-m), $TLOAD =$ Load Torque (N-m), $SPEED = \omega_{mech} = 2\omega_r/P$ (rad/s)

Synchronous RF dq model of a VSI driven IM

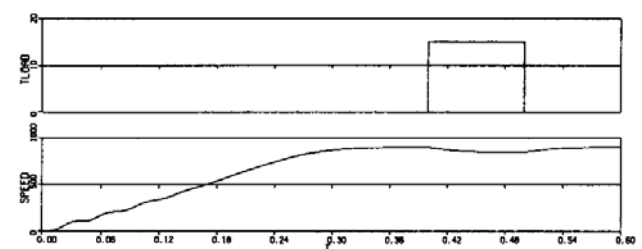
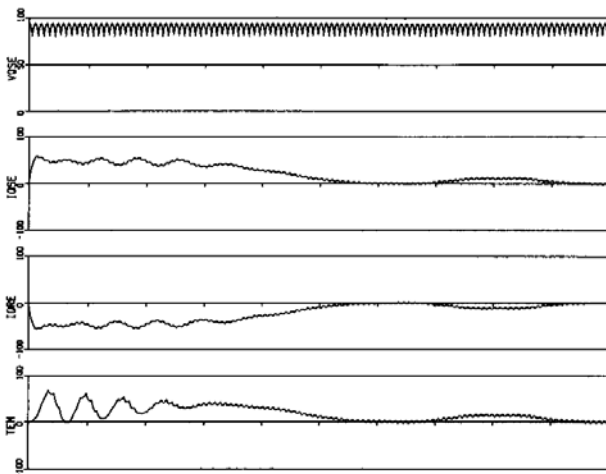


Figure 3.17 Simulation of an induction machine accelerating from rest with a VSI supply with the system represented in the synchronous reference frame. The inverter frequency is fixed at 30 Hz. $VQSE = v_{qs}^e$ (V), $IDSE = i_{ds}^e$ (A), $IQRE = i_{dr}^e$ (A), $TEM = T_e$, (N-m), $TLOAD = T_{load}$ (N-m), $SPEED = (2\omega_r)/P$ rad/s

Synchronous RF dq model of a VSI driven IM (Neglecting the inverter harmonics)

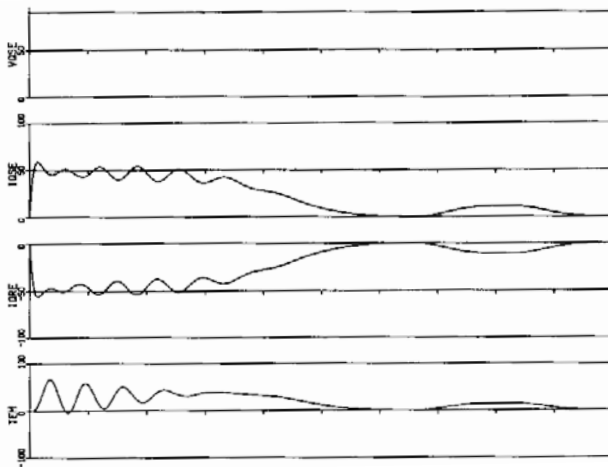


Figure 3.18 Simulation of an induction machine accelerating from rest with a VSI supply with the system represented in the synchronous reference frame neglecting the effect of the inverter harmonics. The inverter frequency is fixed at 30 Hz. $VDSE = v_{ds}^e$ (V), $VQSE = v_{qs}^e$ (V), $IDSE = i_{ds}^e$ (A), $IQSE = i_{qs}^e$ (A), $IQRE = i_{qr}^e$ (A), $TEM = T_e$ (N-m), $SPEED = (2\omega_r)/P$ rad/s

Synchronous RF dq model of a VSI driven IM (Incorporating the dc link filter)


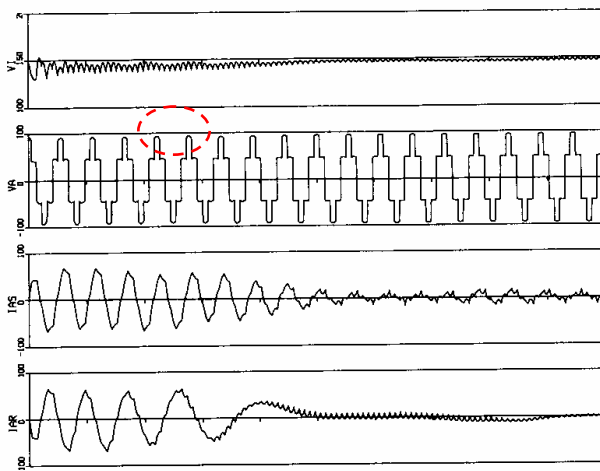


Figure 3.21 Simulation of an induction machine accelerating from rest with an voltage source inverter supply. Simulation incorporates the effect of the dc link filter. The inverter frequency is fixed at 30 Hz. $VI = V_i$ (V), $VA = v_{as} = v_{qs}^s$ (V), $IA = i_{as} = i_{qs}^s$ (A), $IAR = i_{ar}^s$ (A), $TEM = T_e$ (N-m), $TLOAD = T_{load}$ (N-m), $SPEED = (2\omega_r)/P$ (rad/s)

3.7 Fundamental Component Approx. for Steady-State Operation

Fig. 3.24 Output waveforms for basic inverters with constant dc input

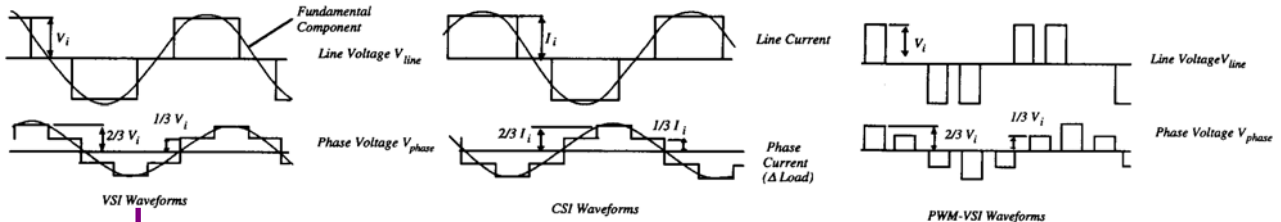

$$v_{line} (= v_{bc}) = \frac{2\sqrt{3}}{\pi} V_i \left[\cos\theta - \frac{1}{5} \cos 5\theta - \frac{1}{7} \cos 7\theta + \frac{1}{11} \cos 11\theta + \dots \right] \quad (3.7-1)$$

$$v_{phase} (= v_{as}) = \frac{2}{\pi} V_i \left[\sin\theta + \frac{1}{5} \sin 5\theta - \frac{1}{7} \sin 7\theta - \frac{1}{11} \sin 11\theta + \dots \right] \quad (3.7-2)$$

$$i_{line} (= i_{as}) = \frac{2\sqrt{3}}{\pi} I_i \left[\cos\theta - \frac{1}{5} \cos 5\theta - \frac{1}{7} \cos 7\theta + \frac{1}{11} \cos 11\theta + \dots \right] \quad (3.7-3)$$

$$i_{phase} (= i_{bc}) = \frac{2}{\pi} I_i \left[\sin\theta + \frac{1}{5} \sin 5\theta - \frac{1}{7} \sin 7\theta - \frac{1}{11} \sin 11\theta + \dots \right] \quad (3.7-4)$$

ai: depends on the mi

$$v_{phase} = \frac{2}{\pi} V_i \left[a_1 \sin\theta_1 + \frac{a_5}{5} \sin\theta_5 - \frac{a_7}{7} \sin\theta_7 + \frac{a_{11}}{11} \sin\theta_{11} + \dots \right] \quad (3.7-5)$$

Input-output relations of an inverter

$$V_i I_i = 3 V_{phase, rms} I_{line, rms} \cos\phi, \quad \phi = \text{power factor angle} \quad (3.7-12)$$

Six step VSI

$$V_{phase, rms} = \frac{\sqrt{2}}{\pi} V_i \quad (3.7-7)$$

$$I_i = \frac{3\sqrt{2}}{\pi} I_{line, rms} \cos\phi \quad (3.7-13)$$

Six step CSI

$$I_{line, rms} = \frac{\sqrt{6}}{\pi} I_i \quad (3.7-8)$$

$$V_i = \frac{3\sqrt{6}}{\pi} V_{phase, rms} \cos\phi \quad (3.7-14)$$

PWM-VSI

$$V_{phase, rms} = \frac{\sqrt{2}}{\pi} a_1 V_i \quad (3.7-11)$$

$$I_i = \frac{3\sqrt{2}}{\pi} a_1 I_{line, rms} \cos\phi \quad (3.7-15)$$

Equivalent circuit of a six step VSI

$$V_{phase, rms} = \frac{\sqrt{2}}{\pi} V_i \quad (3.7-7)$$

$$I_i = \frac{3\sqrt{2}}{\pi} I_{line, rms} \cos \phi \quad (3.7-13)$$

$$I_{line, rms} \cos \phi = \frac{\pi}{3\sqrt{2}} I_i \quad (3.7-17)$$

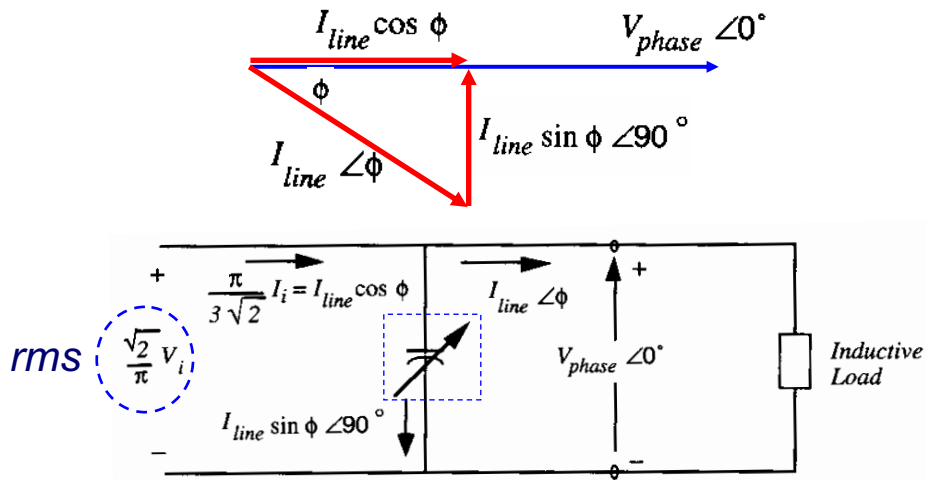


Figure 3.25 Partial per phase fundamental component equivalent circuit of three phase six step VSI

Equivalent circuit of a six step VSI

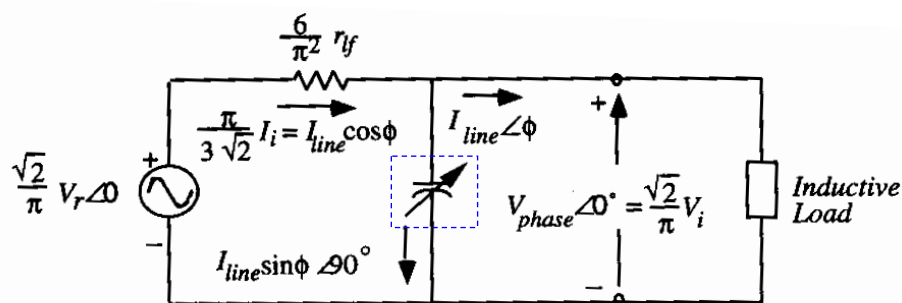


Figure 3.26 Per phase fundamental component equivalent circuit of three phase six step VSI

Equivalent circuit of a six step CSI

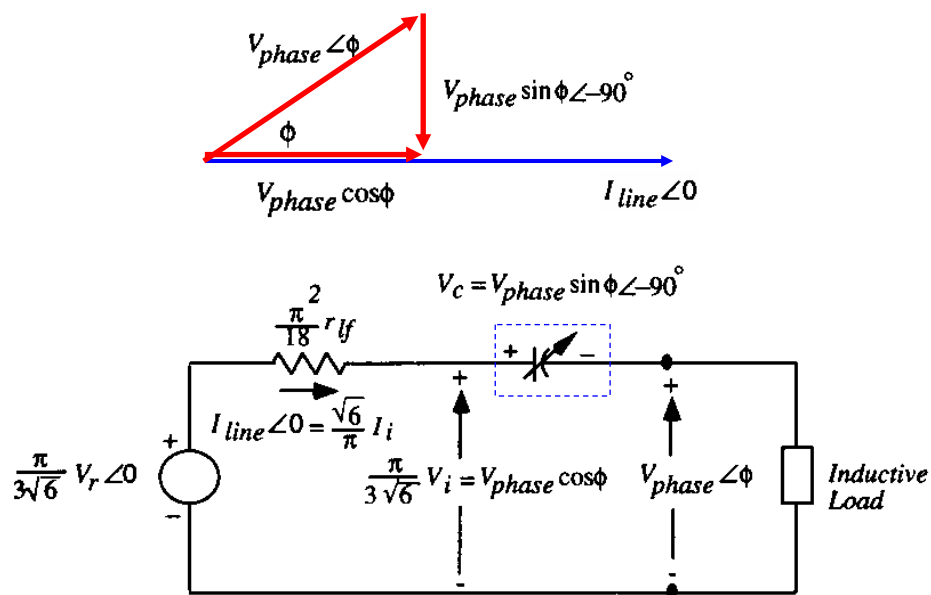


Figure 3.27 Per phase fundamental component equivalent circuit of three phase six step CSI

Equivalent circuit of a PWM-VSI

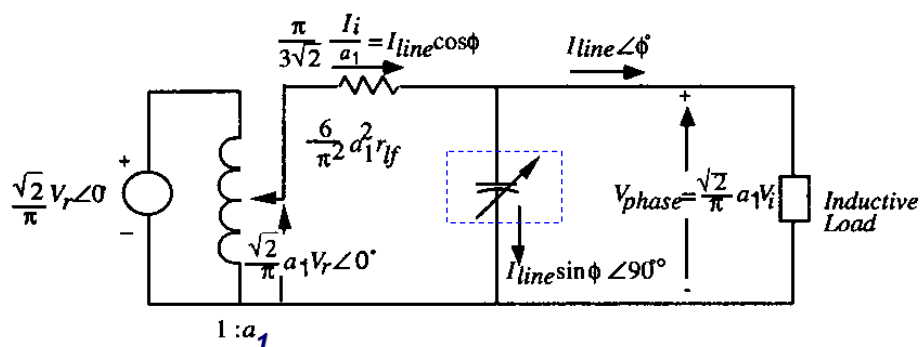


Figure 3.28 Per phase fundamental component equivalent circuit of the three phase PWM-VSI inverter

3.8 Duality of VSI and CSI Systems

Table 3.1 Duality of VSI and CSI Systems

VSI	CSI
1) Output is constrained voltage	1) Output is constrained current
2) dc bus dominated by shunt capacitor	2) dc bus dominated by series inductor
3) dc bus current proportional to motor power and hence dependent on motor power factor	3) dc bus voltage proportional to motor power and hence dependent on motor power factor
4) Output contains voltage harmonics varying inversely as harmonic order	4) Output contains current harmonics varying inversely as harmonic order
5) Prefers motors with larger leakage reactance	5) Prefers motors with lower leakage reactance
6) Can handle motors smaller than inverter rating	6) Can handle motors larger than inverter rating
7) dc bus current reverses in regeneration	7) dc bus voltage reverses in regeneration
8) Immune to open circuits	8) Immune to short circuits